

**Current,**

**Resistance,**

**and**

**Voltage**

**in a simple circuit**


**Part 2**

# Electric Current

Whenever electric charges of like signs move, an *electric current* is said to exist.


Look at the charges flowing perpendicularly to a surface of cross-sectional area  $A$ .

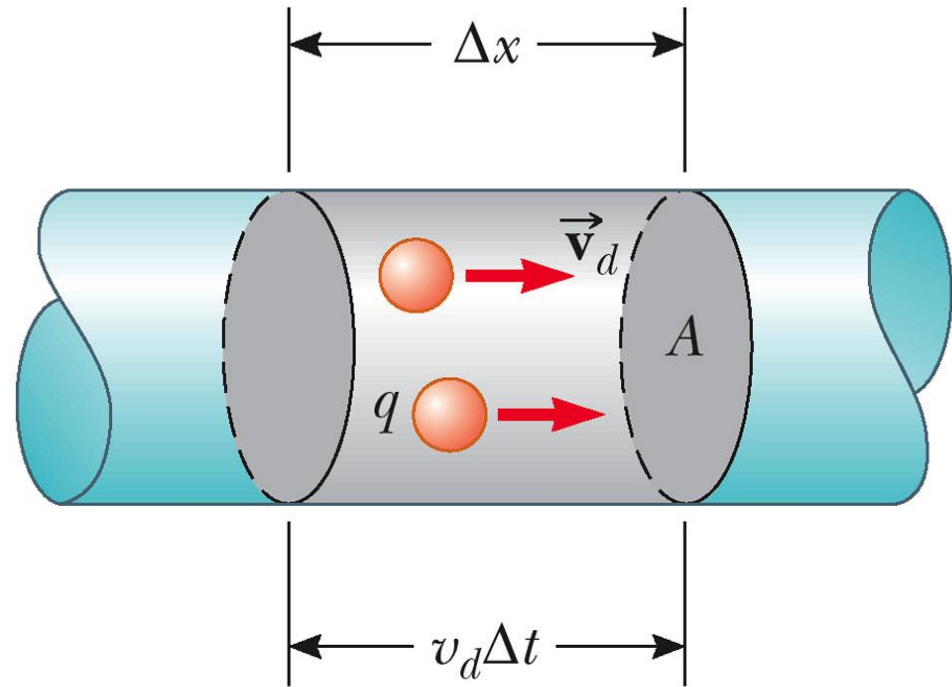(This motion is due to the presence of a uniform electric field along the length of the conductor.)



The current is the rate at which the charge flows through this surface.

$$I \equiv \frac{\Delta Q}{\Delta t}$$

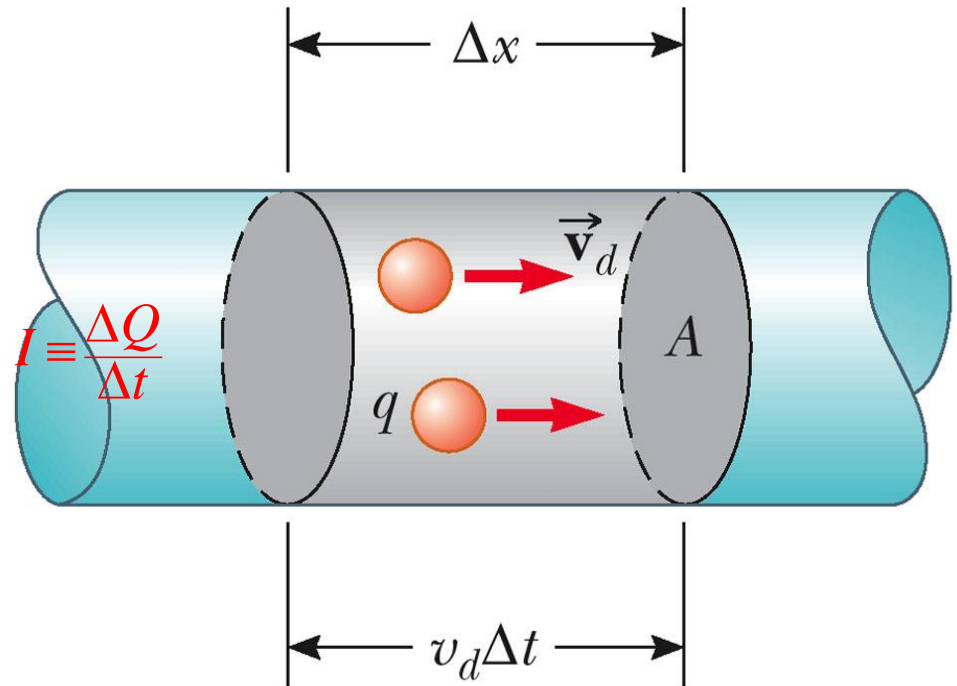

© 2006 Brooks/Cole - Thomson

The SI unit of current is the ampere (A).

$$1 \text{ A} = 1 \text{ C/s}$$

The direction of the current is the direction positive charge would flow.

This is known as *conventional current direction*.

In a common conductor, such as copper, the current is due to the motion of the negatively charged electrons.


It is common to refer to a moving charge as a mobile *charge carrier*.

A charge carrier can be positive or negative
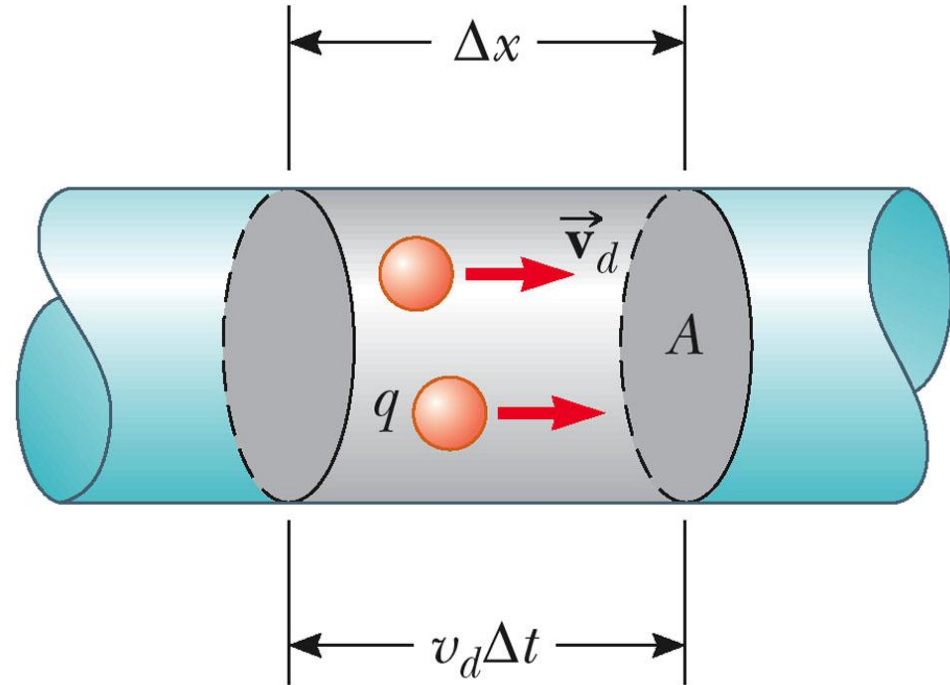
# Current and Drift Speed

$n$  is the number of charge carriers per unit volume.

$nA\Delta x$  is the total number of charge carriers.



# Current and Drift Speed

The total charge is the number of carriers times the charge per carrier,  $q$ .

$$\Delta Q = (nA\Delta x) q$$


The drift speed,  $v_d$ , is the speed at which the carriers move.

$$v_d = \Delta x / \Delta t$$

Rewritten:  $\Delta Q = (nA v_d \Delta t) q$

Finally, current,  $I = \Delta Q / \Delta t = nq v_d A$


# Circuit Elements

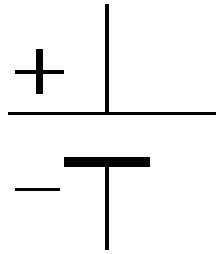

Chemical cell  
e.g., “D” cell



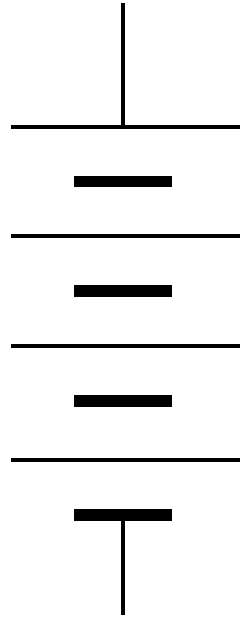Potential difference  
across terminals  $\sim 1.5\text{ V}$




“Battery”  
of cells.




Resistor

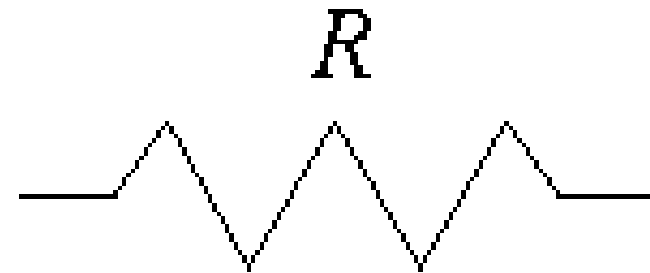Symbolic  
representation  
in a circuit  
diagram



**Connect a battery to a resistor.**  
**Note location and polarity of meters.**

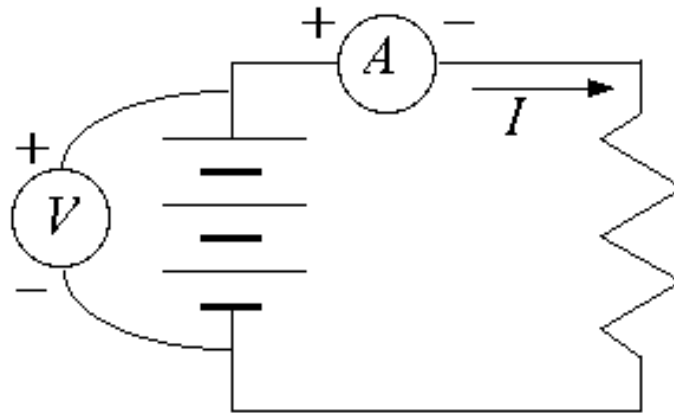**Arrow indicates direction of conventional current.**






For the resistor in this circuit (if temperature is ~ constant), current is proportional to the potential difference across the resistor.

$$I \propto \Delta V \quad \text{or} \quad \Delta V = IR$$

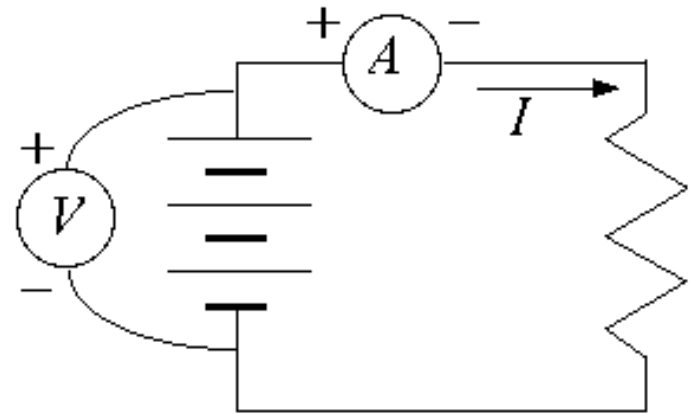This is *Ohm's law* in its simplest form.



The proportionality factor ***R*** is the resistance.  
The unit for resistance is the **ohm** ( $\Omega$ ).

Resistance ( $R$ ) depends upon

- the length  $l$  of the conductor,
- the cross sectional area  $A$ ,
- and the resistivity  $\rho$  of the conductor.

$$R = \rho \frac{l}{A}$$

The unit for resistivity is  $\Omega\text{-m}$ .

The reciprocal of resistance  
is conductance (**G**).

$$G = \frac{1}{R}$$

The unit is  $\Omega^{-1}$ .

The reciprocal of resistivity  
is conductivity ( **$\sigma$** ).

$$\sigma = \frac{1}{\rho}$$

The unit is  $\Omega\text{-m}^{-1}$ .

# **Temperature Variation of Resistivity**

**For most metals, resistivity increases with increasing temperature.**

**With a higher temperature, the metal's constituent atoms vibrate with increasing amplitude.**

**The electrons find it more difficult to pass through the atoms.**

For most metals, resistivity increases approximately linearly with temperature over a limited temperature range.

$$\rho = \rho_0 \left[ 1 + \alpha (T - T_0) \right]$$

$\rho$  is the resistivity at some temperature  $T$ .

$\rho_0$  is the resistivity at some reference temperature  $T_0$ .

$T_0$  is usually taken to be 20° C

$\alpha$  is the temperature coefficient of resistivity.

# Temperature Variation of *Resistance*

Since the resistance of a conductor with uniform cross sectional area is proportional to the resistivity, you can find the effect of temperature on resistance:

$$R = R_o \left[ 1 + \alpha \ T - T_o \right]$$

# Electrical Energy in a Circuit

In a circuit, as a charge moves through the battery, the electrical potential energy of the system is increased by  $\Delta Q \Delta V$ .

The chemical potential energy of the battery decreases by the same amount.


As charge carriers move through a resistor, there is a potential energy loss as the charge carriers collide with atoms in the resistor.

The temperature of the resistor will **increase**.
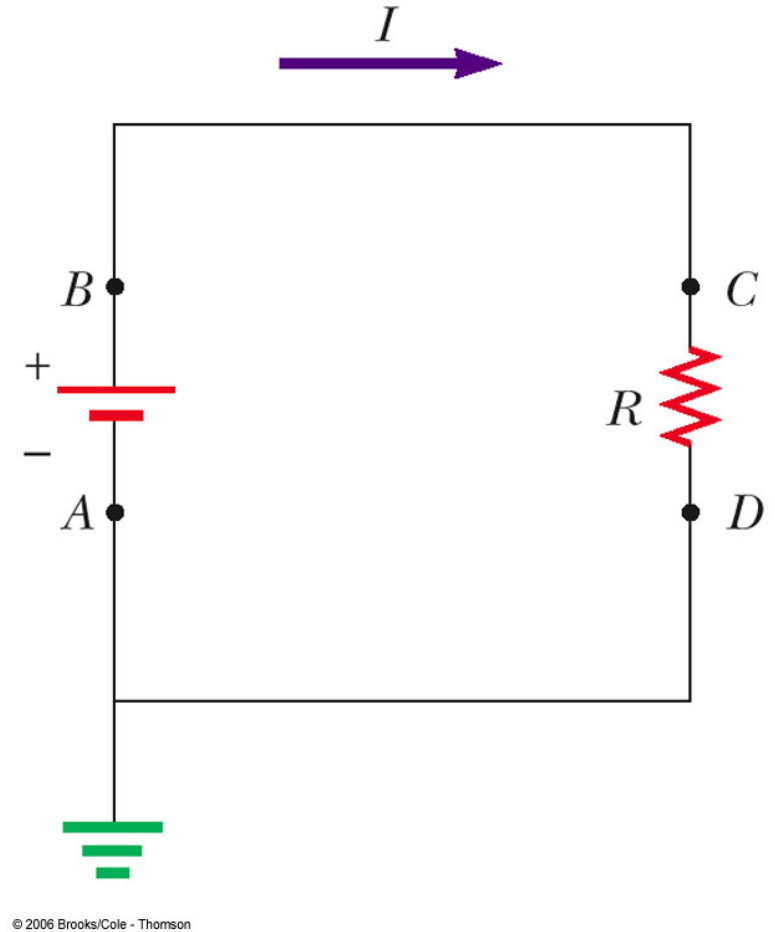
# Energy Transfer in a Circuit

Imagine a quantity of positive charge,  $\Delta Q$ , moving around the circuit along path  $A-B-C-D-A$ .

(If  $R$  is a metal resistor the actual charge movement is electron movement along path  $A-D-C-B-A$ .)






**Point A is the reference point.**

**It is “grounded” and its potential is taken to be zero.**


**As the charge moves through the battery from A to B, the potential energy of the system increases by  $\Delta Q \Delta V$**

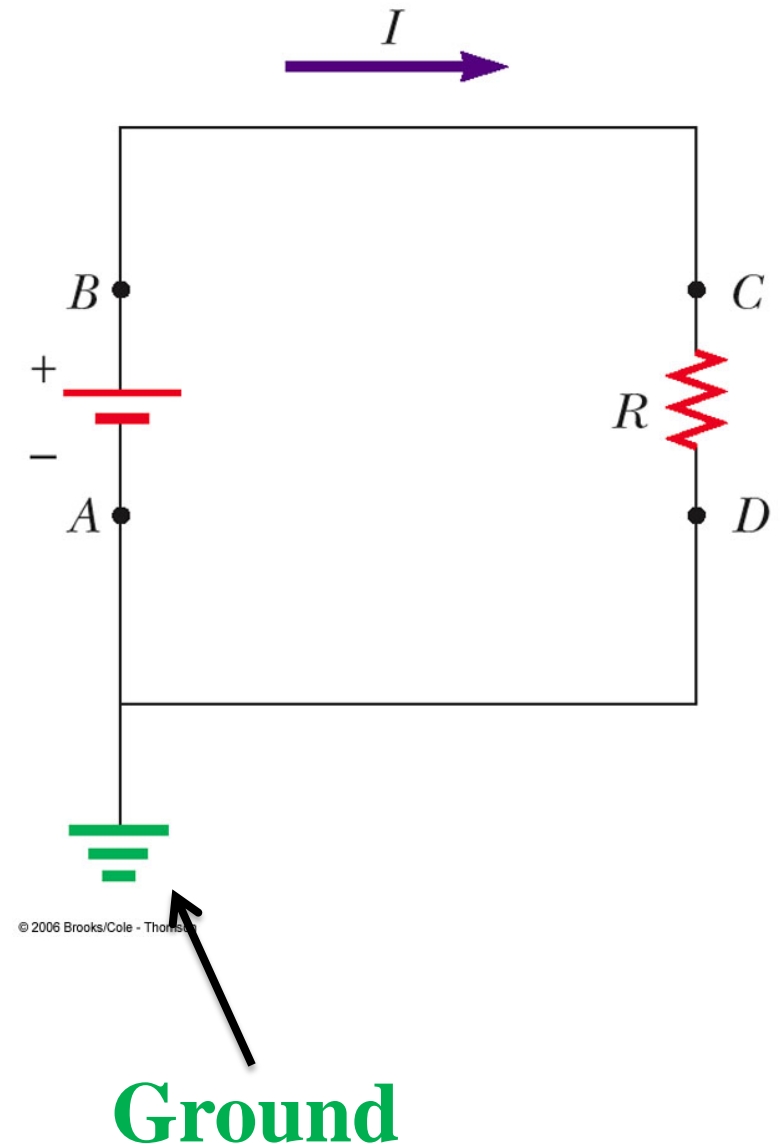**The chemical energy of the battery decreases by the same amount.**



Energy is transferred to **internal energy** of the resistor.

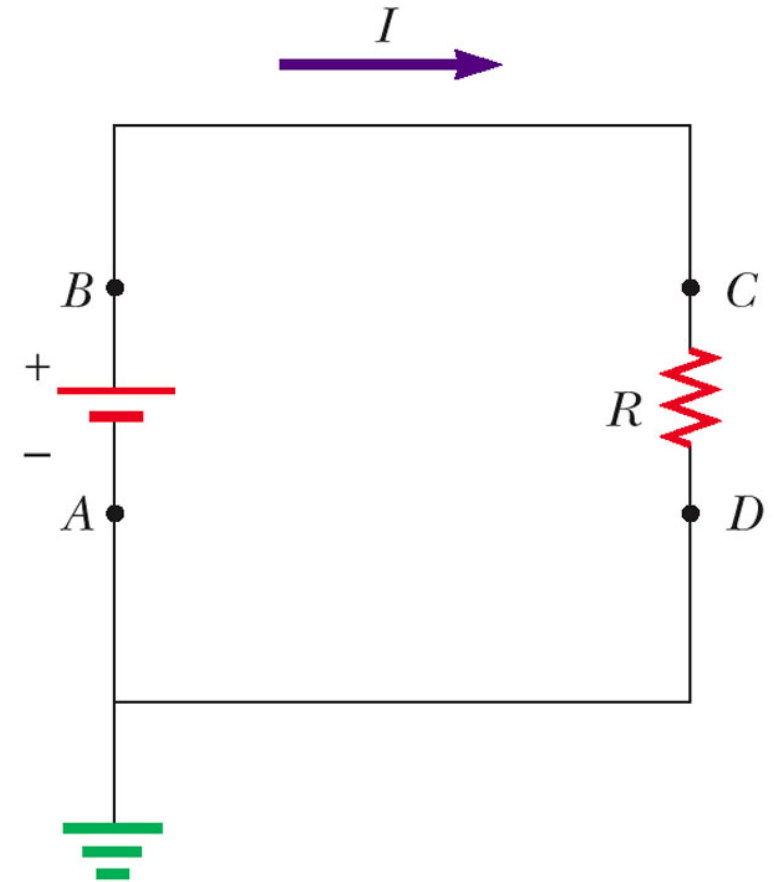When the charge returns to  $A$ , the net result is that some chemical energy of the battery has been delivered to the resistor and caused its temperature to rise.



© 2006 Brooks/Cole - Thomson

# Power

Power is the rate at which energy is delivered to a circuit, or the rate at which energy is dissipated in a circuit.

$$\mathcal{P} = \frac{\Delta Q}{\Delta t} \Delta V = I \Delta V$$

Alternative expressions for power (using Ohm's law):

$$\mathcal{P} = I^2 R = \frac{\Delta V^2}{R}$$

## Units

The SI unit of power is the watt (W)  
 $I$  must be in amperes,  $R$  in ohms and  
 $\Delta V$  in Volts.

The unit of energy used by electric companies  
is the *kilowatt-hour*.

This is defined in terms of the unit of  
power and the amount of time it is  
supplied.

$$1 \text{ kWh} = 3.60 \times 10^6 \text{ J}$$